

Name:

Note: Please post your homework to ICS232 D2L on or before the due date.
If you do not post your homework on or before the due date, please post your late homework when complete (Late Homework: -15% Penalty).

1. (5 pts) Define the following

a. Combination Logic: It is a combination of inputs which lead to output. Two identical inputs into the two logically identical functions will lead to the same output.

b. Sequential Logic: It is the same as combinational Logic except that Sequential Logic has memory.

c. How are sequential circuits different than combinational circuits?
In sequential logic the output is not totally dependent on the input. The output is affected by the memory state.

2. (5 pts) Add the following 8-bit two's complement numbers (i.e. one sign bit and seven data bits) AND indicate "Overflow" if it occurs.

1110 1100 Carry bits

Example: 0101 0110 86
+ 0011 0110 +54

Answer: 0 1000 1100 (-116) 140

Overflow: A Positive Number + a Positive number cannot be a Negative number

a. 1111 0111
+ 1101 0101
Answer: 1001 100

b. 1111 1111
+ 0111 0101
Answer: 1101 00

c. 0110 1111
+ 0101 0101
Answer: 1001 100

overflow when adding the two most significant bits

Name:


3. (5 pts) Construct a truth table for the following:
 $xyz + x(yz)' + x'(y+z) + (xyz)'$

x	y	z	F(xyz)
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

4. (5 pts) Construct a truth table for the following:
 $(x + y')(x' + z')(y' + z')$


x	y	z	F(xyz)
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 5. (5 pts) Construct the XOR operator using only NAND gates. Hint: $x \text{ XOR } y = ((x' y)' (xy')')$




Name:

 6. (5 points) Construct a truth table for a (3) three input XOR gate.



A	B	C	Q
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

7. (5 pts) Given the following circuit:

 

- a. Define the boolean equation for the output function F(xyz)

$$x' + z$$

- b. Define the truth table for the output function F(xyz)

x	y	z	F(xyz)
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Name:

8. (5 pts) Given the truth table below:

A	B	C	Q
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

a. Write out the SOP (Sum-of-Products) minterm Boolean equation.

$$ABC + \bar{A}\bar{B}C + A\bar{B}C + \bar{A}BC$$

b. Construct the K-map for this circuit.

AB	00	01	11	10
C 0				
1	1	1	1	1

$$f(ABC) = C$$

Name:

9. (5 points) Define the deterministic finite automata (DFA) computational model and each term in the quintuple $M=(Q, S, \Sigma, \delta, F)$

DFA model:


$Q: \{A, B, C, D, E, F\}$

$S: \{A\}$

$\Sigma: 0 \text{ or } 1$

$\delta:$

$F: \{F\}$

 

	0	1
A	C	B
B	A	D
C	E	A
D	B	F
E	F	C

10. (5 pts) Define the following terms as they pertain to Latches and Flip-Flops.

Note: The book does not cover these definitions very well. Please visit:

[https://en.wikipedia.org/wiki/Flip-flop_\(electronics\)#JK_flip-flop](https://en.wikipedia.org/wiki/Flip-flop_(electronics)#JK_flip-flop)

- a. Metastability

the horizontal represents time

the vertical portion represents Voltage

When this happens



instead of this



- b. Propagation Delay

It is time slot which separates input time and output time.

- c. Setup Time

Amount of time the input data must remain stable.

This is necessary to prevent input mix up. This is a tool to segregate inputs


- d. Hold Time

Amount of time after clock is active, which

the input data must remain stable. This is necessary to segregate inputs into the correct order of being inputted.

Name:

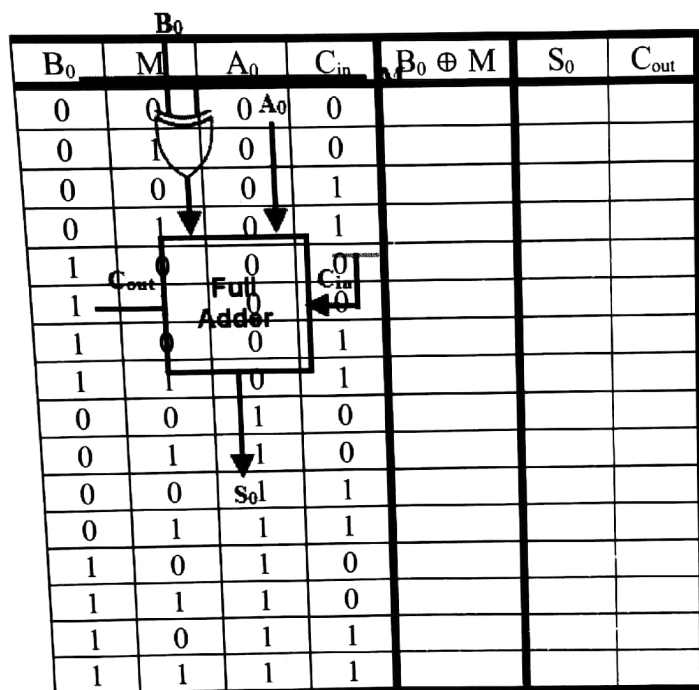
11. (5 pts) Construct the truth table for given the circuit below:




B ₀	M	A ₀	C _{in}	B ₀ ⊕ M	S ₀	C _{out}
0	0	0	0			
0	1	0	0			
0	0	0	1			
0	1	0	1			
1	0	0	0			
1	1	0	0			
1	1	0	1			
1	1	0	1			
0	0	1	0			
0	1	1	0			
0	0	1	1			
0	1	1	1			
1	0	1	0			
1	1	1	0			
1	0	1	1			
1	1	1	1			

Name:

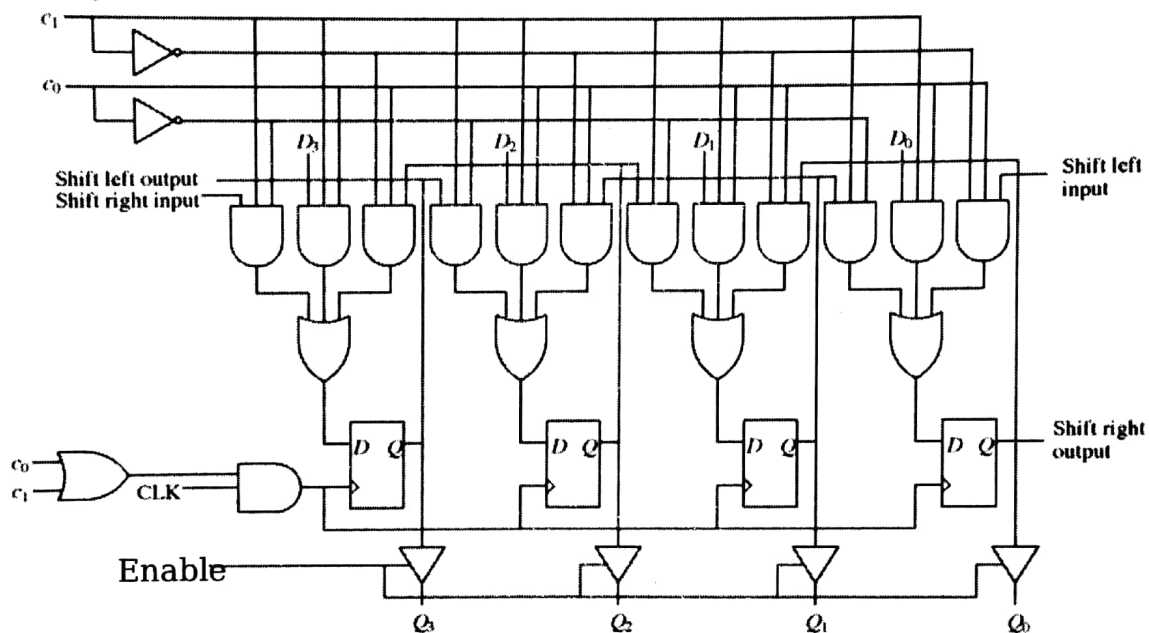12. (5 pts) Given the left-right shift register shown below answer the following questions. Place an 'x' for don't care conditions on the non-relevant outputs.
Note: Each Control input 'c0 and c1' as listed in the function table is shown twice in the diagram.



Control	Function
c ₁ c ₀	
0 0	No change
0 1	Shift left
1 0	Shift right
1 1	Parallel load

 

- a. Fill in the shift output table below for the clocks Clk₁-to-Clk₄ given the following parallel load input to the shift register on clock Clk₀. Place an 'x' for don't care conditions on the non-relevant outputs.

Clk₀

D ₃	D ₂	D ₁	D ₀	C ₁	C ₀
1	1	0	1	1	1

Clk₁-to-Clk₄

	Clk ₁	Clk ₂	Clk ₃	Clk ₄	c ₁	c ₀
Shift Right Output					1	0
Shift Left Output						

Name:

- b. Fill in the state output of Q_0 -to- Q_3 on clock Clk_4 given the input 'Enable=1'
AND the following Input serial load of the shift-register in clocks Clk_0 -to- Clk_3

Clk_0 -to- Clk_3

	Clk_0	Clk_1	Clk_2	Clk_3	C_1	C_0
Shift Right Input	0	1	0	0	1	0
Shift Left Input	1	0	1	1		

Clk_4

Q_3	Q_2	Q_1	Q_0	C_1	C_0	Enable
				0	0	1